

```
-- full_adder.vhd
-- VHDL file for a full adder: a + b + c_in = c_out sum
-- e.g. for a=0, b=1, c_in=1: 0+1+1 = 10
```

```
entity full_adder is
  port(
    a, b, c_in  : IN std_logic;
    c_out, sum : out std_logic);
end full_adder;
```

```
architecture [name]...
begin
  -- full adder descriptive code
end [name];
```

```
-- parallel_adder_4bit.vhd
library...
use...
```

```
entity parallel_adder_4bit is
  generic (width: integer := 8);
  port(
    a, b      : IN std_logic_vector(width downto 1);
    c_in      : IN std_logic;
    c_out     : out std_logic;
    sum       : out std_logic_vector(width downto 1));
end parallel_adder_4bit;
```

```
arch... arch_name2...
  -- declare the component full_adder here (once)
```

```
component full_adder
  port(
    a, b, c_in : IN std_logic;
    c_out, sum : out std_logic);
end component;
```

```
  signal carry : std_logic_vector(1 to width-1);
begin
```

-- instantiate the component here (once for every instance; four times)

Component instantiation

Method 1: explicit port mapping

```
adder1: full_adder
  PORT MAP(  a      => a(1),
             b      => b(1),
             c_in   => c_in,
             c_out  => carry(1),
             sum    => sum(1));

adder2: full_adder
  PORT MAP(  a      => a(2),
             b      => b(2),
             c_in   => carry(1),
             c_out  => carry(2),
             sum    => sum(2));
```

Method 2: implicit port mapping

```
adder1: full_adder PORT MAP(a(1), b(1), c_in,    carry(1), sum(1));
adder2: full_adder PORT MAP(a(2), b(2), carry(1), carry(2), sum(2));
adder3: full_adder PORT MAP(a(3), b(3), carry(2), carry(3), sum(3));
adder4: full_adder PORT MAP(a(4), b(4), carry(3), c_out,  sum(4));
```

Method 3: use GENERATE statement to create multiple component architecture...

```
signal carry : std_logic_vector(0 to width); -- include carry in and out in signal
component full_adder...                      -- declare full adder component
begin
  carry(0)  <= c_in;    -- Assign carry input and output ports to carry signal
  c_out     <= carry(width);

  adders: for i in 1 to width generate
    adder: full_adder port map (a(i), b(i), carry(i-1), carry(i), sum(i));
  end generate;
end [architecture name];
```